

---

**COMPUTER SCIENCE**

**9608/31**

Paper 3 Written Paper

**October/November 2017**

MARK SCHEME

Maximum Mark: 75

---


**Published**

This mark scheme is published as an aid to teachers and candidates, to indicate the requirements of the examination. It shows the basis on which Examiners were instructed to award marks. It does not indicate the details of the discussions that took place at an Examiners' meeting before marking began, which would have considered the acceptability of alternative answers.


Mark schemes should be read in conjunction with the question paper and the Principal Examiner Report for Teachers.

Cambridge International will not enter into discussions about these mark schemes.

Cambridge International is publishing the mark schemes for the October/November 2017 series for most Cambridge IGCSE<sup>®</sup>, Cambridge International A and AS Level components and some Cambridge O Level components.

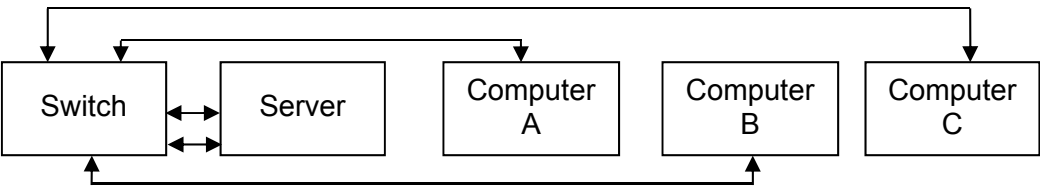Question	Answer	Marks																				
1(a)	 <p data-bbox="296 477 1046 510">Three lines with arrows – one from each device to switch</p>	1																				
1(b)	<table border="1" data-bbox="296 544 1289 965"> <thead> <tr> <th data-bbox="296 544 1026 595">Statement</th> <th data-bbox="1026 544 1158 595">True</th> <th data-bbox="1158 544 1289 595">False</th> <th data-bbox="1289 544 1350 595"></th> </tr> </thead> <tbody> <tr> <td data-bbox="296 595 1026 678">The server can send packets to Computer B and Computer C at the same time.</td> <td data-bbox="1026 595 1158 678">✓</td> <td data-bbox="1158 595 1289 678"></td> <td data-bbox="1289 595 1350 678">1</td> </tr> <tr> <td data-bbox="296 678 1026 761">The network software on each computer needs to include collision detection and avoidance.</td> <td data-bbox="1026 678 1158 761"></td> <td data-bbox="1158 678 1289 761">✓</td> <td data-bbox="1289 678 1350 761">1</td> </tr> <tr> <td data-bbox="296 761 1026 844">Computer B can read the packet sent from the server to Computer C.</td> <td data-bbox="1026 761 1158 844"></td> <td data-bbox="1158 761 1289 844">✓</td> <td data-bbox="1289 761 1350 844">1</td> </tr> <tr> <td data-bbox="296 844 1026 965">Computer A can send a packet to Computer B and at the same time the server can be sending a packet to Computer C.</td> <td data-bbox="1026 844 1158 965">✓</td> <td data-bbox="1158 844 1289 965"></td> <td data-bbox="1289 844 1350 965">1</td> </tr> </tbody> </table>	Statement	True	False		The server can send packets to Computer B and Computer C at the same time.	✓		1	The network software on each computer needs to include collision detection and avoidance.		✓	1	Computer B can read the packet sent from the server to Computer C.		✓	1	Computer A can send a packet to Computer B and at the same time the server can be sending a packet to Computer C.	✓		1	4
Statement	True	False																				
The server can send packets to Computer B and Computer C at the same time.	✓		1																			
The network software on each computer needs to include collision detection and avoidance.		✓	1																			
Computer B can read the packet sent from the server to Computer C.		✓	1																			
Computer A can send a packet to Computer B and at the same time the server can be sending a packet to Computer C.	✓		1																			
1(c)(i)	<p data-bbox="296 999 1334 1227">           Device: <b>Server</b> 1            The server can provide a (software) firewall // The server can check all internet traffic // Server acts as proxy 1            Device: <b>Switch</b> 1            Internet traffic by passes the server // Server not overloaded with internet traffic // connected to all computers 1  <b>1 mark for device, 1 mark for suitable reason</b> </p>	2																				
1(c)(ii)	<ul data-bbox="320 1267 1289 1581" style="list-style-type: none"> <li>• Router acts as gateway</li> <li>• Router acts as a firewall</li> <li>• The LAN and the Internet are two different networks</li> <li>• (may) operate on different protocols</li> <li>• Router forwards packets between networks</li> <li>• Router has a public IP address</li> <li>• Router holds a list of local addresses</li> <li>• Router translates local addresses to Internet (IP) addresses (and vice versa)</li> </ul> <p data-bbox="951 1581 1334 1615"><b>1 mark for each point, max 2</b></p>	2																				
1(c)(iii)	<ul data-bbox="320 1653 1238 1854" style="list-style-type: none"> <li>• Each packet has the IP address of the web server / destination address</li> <li>• The routers use routing tables</li> <li>• Routers on the Internet forward packets towards destination</li> <li>• Packets can take different routes from source to destination</li> <li>• Packets are reassembled in order at the web server</li> </ul> <p data-bbox="951 1854 1334 1888"><b>1 mark for each point, max 3</b></p>	3																				

Question	Answer	Marks										
2(a)	<table border="0" style="width: 100%; border-collapse: collapse;"> <tr> <td style="text-align: center; width: 50%;"><b>Description</b></td> <td style="text-align: center; width: 50%;"><b>Computer architecture</b></td> </tr> <tr> <td style="border: 1px solid black; padding: 5px;">Most parallel computer systems use this architecture.</td> <td style="border: 1px solid black; padding: 5px;">SIMD</td> </tr> <tr> <td style="border: 1px solid black; padding: 5px;">Widely used to process 3D graphics in video games.</td> <td style="border: 1px solid black; padding: 5px;">MIMD</td> </tr> <tr> <td style="border: 1px solid black; padding: 5px;">A microprocessor is used to control a washing machine.</td> <td style="border: 1px solid black; padding: 5px;">MISD</td> </tr> <tr> <td style="border: 1px solid black; padding: 5px;">There are a number of processing units. Each processing unit executes the same instruction but on different data</td> <td style="border: 1px solid black; padding: 5px;">SISD</td> </tr> </table> <p style="text-align: right; margin-top: 10px;">1 mark for each correct line</p>	<b>Description</b>	<b>Computer architecture</b>	Most parallel computer systems use this architecture.	SIMD	Widely used to process 3D graphics in video games.	MIMD	A microprocessor is used to control a washing machine.	MISD	There are a number of processing units. Each processing unit executes the same instruction but on different data	SISD	<b>4</b>
<b>Description</b>	<b>Computer architecture</b>											
Most parallel computer systems use this architecture.	SIMD											
Widely used to process 3D graphics in video games.	MIMD											
A microprocessor is used to control a washing machine.	MISD											
There are a number of processing units. Each processing unit executes the same instruction but on different data	SISD											
2(b)	<ul style="list-style-type: none"> <li>• Only one (separate) processor / not many separate processors (is not massively parallel) <span style="float: right;">1</span></li> <li>• Quad core computer system // processing units share the same bus <span style="float: right;">1</span></li> </ul> <p style="text-align: right;"><b>1 mark for each point, max 2</b></p>	<b>2</b>										
2(c)	<ul style="list-style-type: none"> <li>• Split into blocks of code ....</li> <li>• ... that can be processed simultaneously ...</li> <li>• ... instead of sequentially</li> <li>• Each block is processed by a different processor</li> <li>• which allows each of the many processors to simultaneously process the different blocks of code independently</li> <li>• Requires both parallelism and co-ordination</li> </ul> <p style="text-align: right;"><b>1 mark for each point, max 2</b></p>	<b>2</b>										
2(d)	<p><b>1 mark</b> for identification of hardware issue, for example:</p> <ul style="list-style-type: none"> <li>• Communication between the different processors is the issue</li> </ul> <p><b>1 mark</b> for further explanation from:</p> <ul style="list-style-type: none"> <li>• Each processor needs a link to every other processor</li> <li>• Many processors require many of these links</li> <li>• Challenging topology</li> </ul>	<b>2</b>										

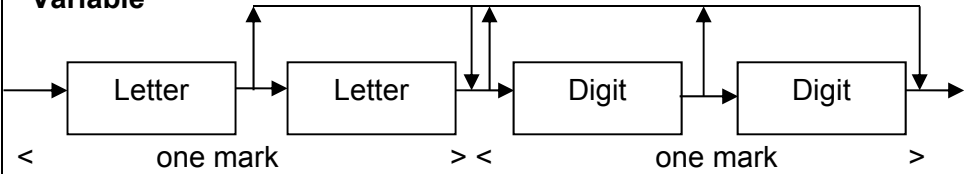Question	Answer	Marks
3(a)(i)	There should be a colon before the '=' sign	1
3(a)(ii)	The second operand should be an unsigned integer and not a variable	1
3(a)(iii)	A32 is not a variable, as a variable should be a letter followed by a single digit	1
3(b)	<pre> &lt;assignment_statement&gt; ::= &lt;variable&gt; := &lt;variable&gt; &lt;operator&gt; &lt;unsigned_integer&gt; &lt;variable&gt; ::= &lt;letter&gt; &lt;digit&gt; &lt;unsigned_integer&gt; ::= &lt;digit&gt;   &lt;digit&gt; &lt;unsigned_integer&gt; &lt;letter&gt; ::= A   B   C &lt;operator&gt; ::= +   -   *   ^                     </pre>	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p>
3(c)	<p><b>Variable</b></p>  <p>Syntax diagram shows one or two letters</p> <p>Syntax diagram shows zero, one or two digits</p>	<p>2</p> <p>1</p> <p>1</p>
3(d)	<pre> &lt;assignment_statement&gt; ::= &lt;variable&gt; := &lt;variable&gt; &lt;operator&gt; &lt;real&gt; &lt;real&gt; ::= &lt;unsigned_integer&gt; . &lt;unsigned_integer&gt;                     </pre>	<p>2</p> <p>1</p> <p>1</p>

Question	Answer	Marks
4(a)(i)	A (known) set of rules Agreed/standard method for data transmission // governs how two devices communicate	1 1 <b>2</b>
4(a)(ii)	<b>Max 2 marks</b> for purpose: <ul style="list-style-type: none"> <li>• Purpose of TLS is to provide for secure communication (over a network)</li> <li>• maintain data integrity</li> <li>• additional layer of security</li> </ul> <b>Max 2 marks</b> for further explanation from: <ul style="list-style-type: none"> <li>• TLS provides improved security over SSL</li> <li>• TLS is composed of two layers / record protocol and handshake protocol</li> <li>• TLS protects this information by using encryption</li> <li>• Also allows for authentication of servers and clients</li> </ul>	<b>Max 3</b>
4(b)	<ul style="list-style-type: none"> <li>• The client validates (the server's) TLS Certificate</li> <li>• The client sends its digital certificate (to the server if requested)</li> <li>• Client sends an encrypted message to the server using the server's public key</li> <li>• The server can use its private key to decrypt the message ...</li> <li>• ... and get data needed for generating symmetric key</li> <li>• Both server and client compute symmetric key (to be used for encrypting messages) // session key established</li> <li>• The client sends back a digitally signed acknowledgement to start an encrypted session</li> <li>• The server sends back a digitally signed acknowledgement to start an encrypted session</li> </ul> <p style="text-align: right;"><b>1 mark</b> for each point, <b>max 3</b> points</p>	<b>3</b>
4(c)	Applications, for example: <ul style="list-style-type: none"> <li>• online banking</li> <li>• private email</li> <li>• online shopping</li> <li>• online messaging etc.</li> </ul> <p style="text-align: right;"><b>1 mark</b> for each point, <b>Max 2</b></p>	<b>2</b>

Question	Answer	Marks															
5(a)(i)	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	<b>1</b>
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

Question	Answer	Marks																																																																												
5(a)(ii)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	C	X	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	<b>1</b>																																								
A	B	C	X																																																																											
0	0	0	1																																																																											
0	0	1	1																																																																											
0	1	0	1																																																																											
0	1	1	1																																																																											
1	0	0	1																																																																											
1	0	1	1																																																																											
1	1	0	1																																																																											
1	1	1	0																																																																											
5(b)(i)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th></th> <th>S</th> <th>R</th> <th>Q</th> <th><math>\bar{Q}</math></th> <th></th> </tr> </thead> <tbody> <tr> <td>Initially</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>R changed to 1</td> <td>1</td> <td>1</td> <td><b>0</b></td> <td><b>1</b></td> <td>1</td> </tr> <tr> <td>S changed to 0</td> <td>0</td> <td>1</td> <td><b>1</b></td> <td><b>0</b></td> <td>1</td> </tr> <tr> <td>S changed to 1</td> <td>1</td> <td>1</td> <td><b>1</b></td> <td><b>0</b></td> <td>1</td> </tr> <tr> <td>S and R changed to 0</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>		S	R	Q	$\bar{Q}$		Initially	1	0	0	1		R changed to 1	1	1	<b>0</b>	<b>1</b>	1	S changed to 0	0	1	<b>1</b>	<b>0</b>	1	S changed to 1	1	1	<b>1</b>	<b>0</b>	1	S and R changed to 0	0	0	1	1		<b>3</b>																																								
	S	R	Q	$\bar{Q}$																																																																										
Initially	1	0	0	1																																																																										
R changed to 1	1	1	<b>0</b>	<b>1</b>	1																																																																									
S changed to 0	0	1	<b>1</b>	<b>0</b>	1																																																																									
S changed to 1	1	1	<b>1</b>	<b>0</b>	1																																																																									
S and R changed to 0	0	0	1	1																																																																										
5(b)(ii)	<ul style="list-style-type: none"> <li>• Q and <math>\bar{Q}</math> have same value</li> <li>• Q and <math>\bar{Q}</math> should be complements of each other</li> <li>• Flip-flop becomes unstable</li> </ul> <p style="text-align: right;"><b>1 mark for each point, max 2</b></p>	<b>2</b>																																																																												
5(c)(i)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th rowspan="2">J</th> <th rowspan="2">K</th> <th rowspan="2">Clock</th> <th rowspan="2">Working space</th> <th colspan="2">Initial values</th> <th colspan="2">Final values</th> </tr> <tr> <th>Q</th> <th><math>\bar{Q}</math></th> <th>Q</th> <th><math>\bar{Q}</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td><b>1</b></td><td><b>0</b></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td><b>1</b></td><td><b>0</b></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td><b>0</b></td><td><b>1</b></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td><b>1</b></td><td><b>0</b></td></tr> </tbody> </table> <p style="text-align: right;">1 mark per shaded row</p>	J	K	Clock	Working space	Initial values		Final values		Q	$\bar{Q}$	Q	$\bar{Q}$	0	0	1		1	0	1	0	0	0	1		0	1	0	1	0	1	1		1	0	0	1	0	1	1		0	1	0	1	1	0	1		1	0	<b>1</b>	<b>0</b>	1	0	1		0	1	<b>1</b>	<b>0</b>	1	1	1		1	0	<b>0</b>	<b>1</b>	1	1	1		0	1	<b>1</b>	<b>0</b>	<b>4</b>
J	K					Clock	Working space	Initial values		Final values																																																																				
		Q	$\bar{Q}$	Q	$\bar{Q}$																																																																									
0	0	1		1	0	1	0																																																																							
0	0	1		0	1	0	1																																																																							
0	1	1		1	0	0	1																																																																							
0	1	1		0	1	0	1																																																																							
1	0	1		1	0	<b>1</b>	<b>0</b>																																																																							
1	0	1		0	1	<b>1</b>	<b>0</b>																																																																							
1	1	1		1	0	<b>0</b>	<b>1</b>																																																																							
1	1	1		0	1	<b>1</b>	<b>0</b>																																																																							
5(c)(ii)	<ul style="list-style-type: none"> <li>• S-R flip-flop has an invalid combination of S and R // The S_R flip flop allows both Q and <math>\bar{Q}</math> to have the same value // S-R flip-flop inputs may arrive at different times <span style="float: right;">1</span></li> <li>• The J-K flip-flop does not allow for Q and <math>\bar{Q}</math> to have the same value // All four combination of values for J and K are valid // J-K flip-flop incorporates a clock pulse for synchronisation <span style="float: right;">1</span></li> </ul>	<b>2</b>																																																																												

Question	Answer	Marks
5(d)	<ul style="list-style-type: none"> <li>• A flip-flop can store either a 0 or a 1</li> <li>• Computers use bits to store data</li> <li>• Flip-flops can therefore be used to store bits (of data)</li> <li>• Memory can be created from flip-flops</li> </ul> <p style="text-align: right;"><b>1 mark for valid point, max 2</b></p>	<b>2</b>

Question	Answer	Marks																																																																																
6(a)(i)	Control system	<b>1</b>																																																																																
6(a)(ii)	System is controlling devices // turns heaters on and off // use of actuators maintain the environment // makes use of feedback	<b>1</b>																																																																																
6(b)	Computer/microprocessor ... to process the sensor readings Analogue to digital convertor ... <u>Sensor</u> produces analogue signal but processor requires digital data Digital to analogue convertor ... <u>Processor</u> produces digital signal but actuator may require analogue sign Actuator ... May be required to turn heater on or off <p style="text-align: right;"><b>1 mark for device, 1 mark for justification, max 2 devices</b></p>	<b>4</b>																																																																																
6(c)(i)	One mark per column excluding LOWTEMP <table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <thead> <tr> <th>LOWTEMP</th> <th>LOWREG</th> <th>COUNTER</th> <th>ACC</th> <th>IX</th> </tr> </thead> <tbody> <tr> <td>15</td> <td>B00000000</td> <td>1</td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> <td>0</td> </tr> <tr> <td></td> <td></td> <td></td> <td>17</td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td>1</td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td>2</td> <td></td> </tr> <tr> <td></td> <td></td> <td>2</td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> <td>1</td> </tr> <tr> <td></td> <td></td> <td></td> <td>14</td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td>B00000000</td> <td></td> </tr> <tr> <td></td> <td>B00000010</td> <td></td> <td>B00000010</td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td>2</td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td>4</td> <td></td> </tr> <tr> <td></td> <td></td> <td>4</td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> <td>2</td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>	LOWTEMP	LOWREG	COUNTER	ACC	IX	15	B00000000	1							0				17					1					2				2							1				14					B00000000			B00000010		B00000010					2					4				4							2						<b>4</b>
LOWTEMP	LOWREG	COUNTER	ACC	IX																																																																														
15	B00000000	1																																																																																
				0																																																																														
			17																																																																															
			1																																																																															
			2																																																																															
		2																																																																																
				1																																																																														
			14																																																																															
			B00000000																																																																															
	B00000010		B00000010																																																																															
			2																																																																															
			4																																																																															
		4																																																																																
				2																																																																														
6(c)(ii)	<ul style="list-style-type: none"> <li>• COUNTER has an initial value of 1</li> <li>• Test for final value is before COUNTER updated</li> <li>• COUNTER is doubled in value each time around loop</li> <li>• six sensors values/bits to check</li> <li>• COUNTER is doubled in value 6 times // <math>2^5</math></li> <li>• Values of COUNTER at test will therefore be 1 – 2 – 4 – 8 – 16 – 32</li> </ul> <p style="text-align: right;"><b>1 mark for valid point, max 2</b></p>	<b>2</b>																																																																																

Question	Answer	Marks
6(c)(iii)	<ul style="list-style-type: none"><li>• Load the contents of <code>LOWREG</code> into <code>ACC</code></li><li>• Check bit position in <code>LOWREG</code></li><li>• For each of the least significant 6 bits</li><li>• Use <code>AND</code> operation / mask to isolate a bit</li><li>• Jump to code corresponding to bit being looked at</li><li>• if value of bit is 1</li><li>• Send signal to appropriate actuator to turn on the heater</li></ul> <p style="text-align: right;"><b>1 mark</b> for valid point, <b>max 3</b></p>	<b>3</b>